

Control the Voltage of a Remote Load Over Any Length of Copper Wire – Design Note 529

Philip Karantzalis

Introduction

A common problem in power distribution systems is loss of regulation due to the cable/wire voltage drop between the regulator and the load. Any increase in wire resistance, cable length or load current increases the voltage drop over the distribution wire, increasing the difference between actual voltage at the load and the voltage perceived by the regulator. One way to improve regulation over long cable runs is to measure voltage directly at the load via a 4-wire Kelvin connection between the regulator and the load. Unfortunately, this solution requires routing additional wires to the load as well as a Kelvin resistor placed near the load, impractical when the load is inaccessible for modification. Another method minimizes the voltage drop by employing large diameter wire, lowering the resistance from the regulator to the load. This is electrically simple, but can be mechanically complicated. Increasing the size of cable conductors can significantly increase space requirements and cost.

An alternative to additional wiring is to compensate for the voltage drop at the regulator with the **LT[®]6110** cable/wire drop compensator without additional cabling/wiring between the regulator and load. This article shows how the LT6110 can improve regulation by compensating for a wide range of regulator-to-load voltage drops.

The LT6110 Cable/Wire Compensator

Figure 1 shows a 1-wire compensation block diagram. If the remote load circuit does not share the regulator's ground, two wires are required, one to the load and one ground return wire. The LT6110 high side amplifier senses the load current by measuring the voltage, V_{SENSE} , across the sense resistor, R_{SENSE} , and outputs a current, I_{IOUT} proportional to the load current, I_{LOAD} . I_{IOUT} is programmable with the R_{RIN} resistor from $10\mu A$ to $1mA$. Cable/wire voltage drop, V_{DROP} compensation is accomplished by sinking I_{IOUT} through the R_{FA} feedback resistor to increase the regulator's output by an amount equal to V_{DROP} . An LT6110 cable/wire voltage drop compensation design is simple: set the $I_{IOUT} \cdot R_{FA}$ product equal to the maximum cable/wire voltage drop.

The LT6110 includes an internal $20m\Omega$ R_{SENSE} , suitable for load currents up to $3A$; an external R_{SENSE} is required for I_{LOAD} greater than $3A$. The external R_{SENSE} can be a sense resistor, the DC resistance of an inductor or a PCB trace resistor. In addition to the I_{IOUT} sink current, the LT6110 I_{MON} pin provides a sourcing current, I_{MON} , to compensate current-referenced linear regulators such as the **LT3080**.

LT, LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

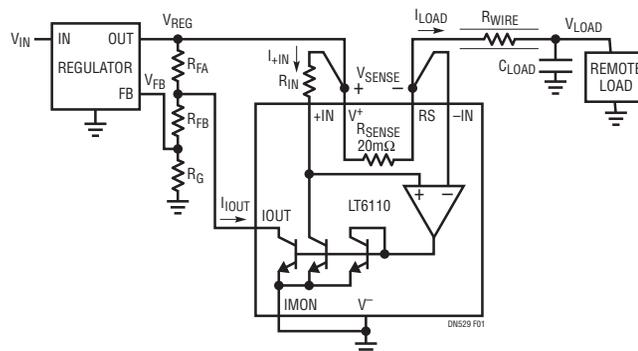


Figure 1. No Extra Wires Are Required to Compensate for Wire Voltage Drop to a Remote Load

Compensating Cable Voltage Drops for a Buck Regulator

Figure 2 shows a complete cable/wire voltage drop compensation system consisting of a 3.3V, 5A buck regulator and an LT6110, which regulates the voltage of a remote load connected through 20 feet of 18 AWG copper wire. The buck regulator's 5A output requires the use of an external R_{SENSE} .

The maximum 5A I_{LOAD} through the 140m Ω wire resistance and 25m Ω R_{SENSE} creates an 825mV voltage drop. To regulate the load voltage, V_{LOAD} , for $0A \leq I_{LOAD} \leq 5A$, $I_{IOUT} \cdot R_{FA}$ must equal 825mV. There are two design options: select I_{IOUT} and calculate the R_{FA} resistor, or design the regulator's feedback resistors for very low current and calculate the R_{IN} resistor to set I_{IOUT} . Typically I_{IOUT} is set to 100 μ A (the I_{IOUT} error is $\pm 1\%$ from 30 μ A to 300 μ A). In the Figure 2 circuit, the feedback path current is 6 μ A ($V_{FB}/200k$), the R_{FA} resistor is 10k and the R_{IN} resistor must be calculated to set $I_{IOUT} \cdot R_{FA} = 825mV$.

$$I_{IOUT} = V_{SENSE}/R_{IN}, I_{IOUT} \cdot R_{FA} = V_{DROP}$$

and

$$R_{IN} = R_{FA} \cdot \frac{R_{SENSE}}{R_{SENSE} \cdot R_{WIRE}}$$

and

for $R_{FA} = 10k$, $R_{SENSE} = 25m\Omega$ and $R_{WIRE} = 140m\Omega$, $R_{IN} = 1.5k$.

Without cable/wire drop compensation the maximum change in load voltage, ΔV_{LOAD} , is 700mV ($5 \cdot 140m\Omega$), or an error of 21.2% for a 3.3V output. The LT6110 reduces ΔV_{LOAD} to only 50mV at 25 $^{\circ}$ C, or an error of 1.5%. This is an order of magnitude improvement in load regulation.

Precision Load Regulation


A modest improvement in load regulation with the LT6110 does not require accurate R_{WIRE} estimation. The load regulation error is the product of two errors: error due to the wire/cable resistance and error due to the LT6110 compensation circuit. For example, using the Figure 2 circuit, even if the R_{SENSE} and R_{WIRE} calculation error is 25%, the LT6110 still reduces V_{LOAD} error to 6.25%.

For precise load regulation, an accurate estimate of the resistance between the power source and load is required. If R_{WIRE} , R_{SENSE} and the resistance of the cable connectors and PCB traces in series with the wire is accurately estimated, then the LT6110 can compensate for a wide range of voltage drops to a high degree of precision.

Using the LT6110, an accurate R_{WIRE} estimation and a precision R_{SENSE} , the ΔV_{LOAD} compensation error can be reduced to match the regulator's voltage error over any length of wire.

Conclusion

The LT6110 cable/wire voltage drop compensator improves the voltage regulation of remote loads, where high current, long cable runs and resistance would otherwise significantly affect regulation. Accurate regulation can be achieved without adding sense wires, buying Kelvin resistors, using more copper or implementing point-of-load regulators—common drawbacks of other solutions. In contrast, compensator solutions require little space while minimizing design complexity and component costs.

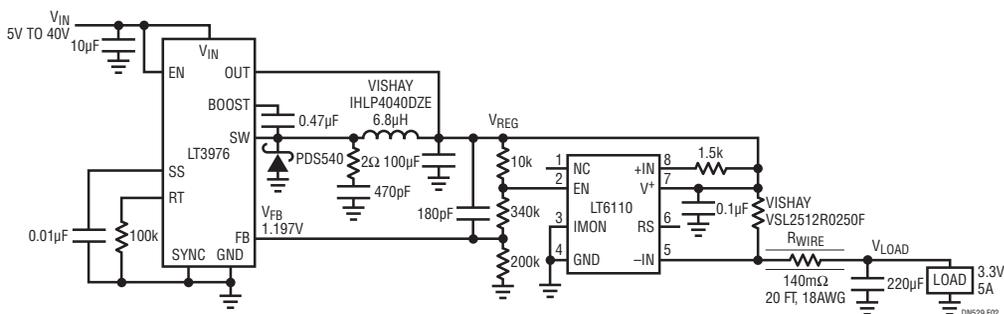

**Figure 2. Example of a High Current Remote Load Regulation:
A 3.3V, 5A Buck Regulator with LT6110 Cable/Wire Voltage Drop Compensation**

Data Sheet Download

www.linear.com/LT6110

For applications help,
call (408) 432-1900, Ext. 3761

Linear Technology Corporation
1630 McCarthy Blvd., Milpitas, CA 95035-7417
(408) 432-1900 • FAX: (408) 434-0507 • www.linear.com

dn529f LT/AP 0814 111K • PRINTED IN THE USA


© LINEAR TECHNOLOGY CORPORATION 2014